

4: Linearity and Superposition

Linearity Theorem

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.


(1) Label all the nodes

(2) KCL equations:

$$\frac{X - U_1}{2} + \frac{X}{1} + \frac{X - Y}{3} = 0 \quad \frac{Y - X}{3} + (-U_2) = 0$$

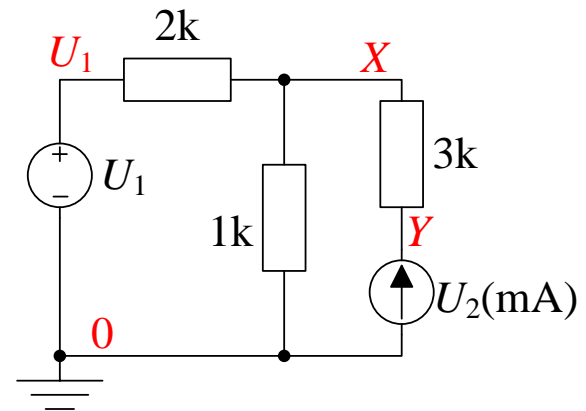(3) Solve for the node voltages:

$$X = \frac{1}{2}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$




Steps (2) and (3) never involve multiplying two source values together, so:

Linearity Theorem: For any circuit containing resistors and independent voltage and current sources, every node voltage and branch current is a linear function of the source values and has the form $\sum a_i U_i$ where the U_i are the source values and the a_i are suitably dimensioned constants.


Also true for a circuit containing *dependent* sources whose values are proportional to voltages or currents elsewhere in the circuit.

Zero-value Sources

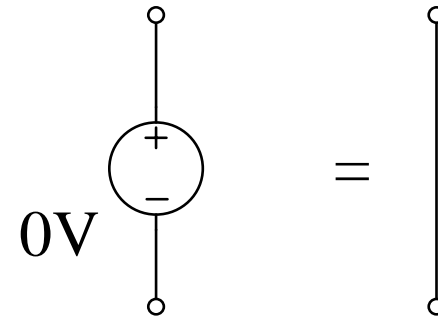A **zero-valued** voltage source has zero volts between its terminals for any current. It is equivalent to a **short-circuit** or a piece of wire or a resistor of 0Ω (or ∞S)



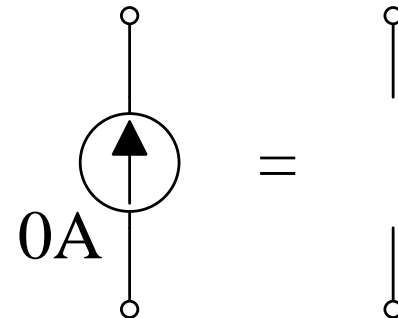A **zero-valued** current source has no current flowing between its terminals. It is equivalent to an **open-circuit** or a broken wire or a resistor of $\infty \Omega$ (or $0 S$)




Superposition

We can use nodal analysis to find X in terms of U , V and W .




$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

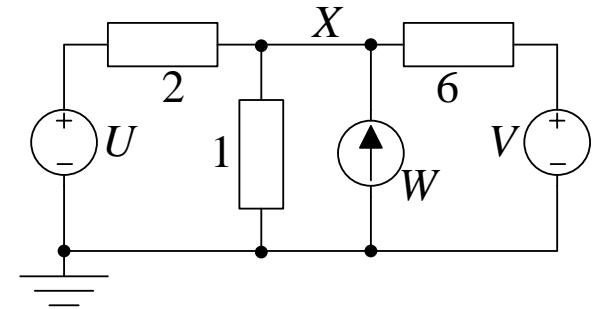

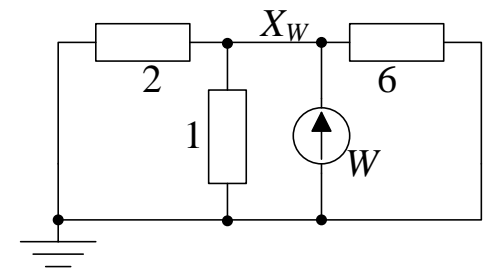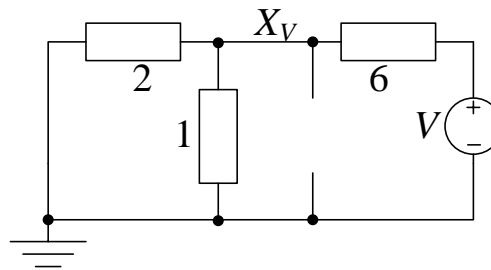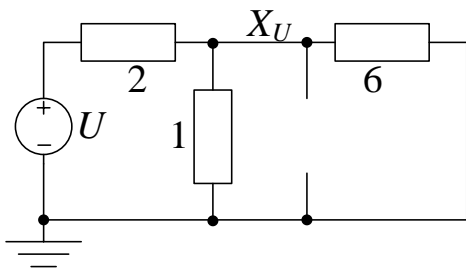From the linearity theorem, we know anyway that $X = aU + bV + cW$ so all we need to do is find the values of a , b and c . We find each coefficient in turn by setting all the other sources to zero:




From the LH diagram we have $X_U = aU + b \times 0 + c \times 0 = aU$.


Similarly, $X_V = bV$ and $X_W = cW \Rightarrow X = X_U + X_V + X_W$.

Superposition Calculation

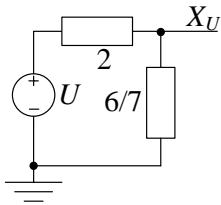
Method: Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


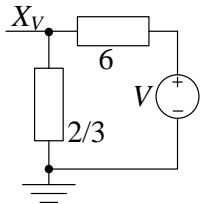
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$



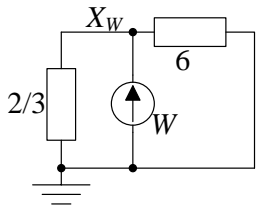
$$X_V = \frac{\frac{2}{3}}{6 + \frac{2}{3}} V = \frac{2}{20} V = 0.1V$$



$$X_W = \frac{6}{6 + \frac{2}{3}} W \times \frac{2}{3} = \frac{12}{20} W = 0.6W$$

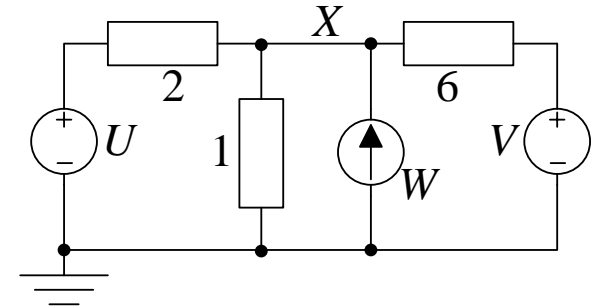Adding them up: $X = X_U + X_V + X_W = 0.3U + 0.1V + 0.6W$




Superposition and Dependent Sources

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here $V \triangleq Y - X$.

Step 1: Pretend all sources are independent and use superposition to find expressions for the node voltages:
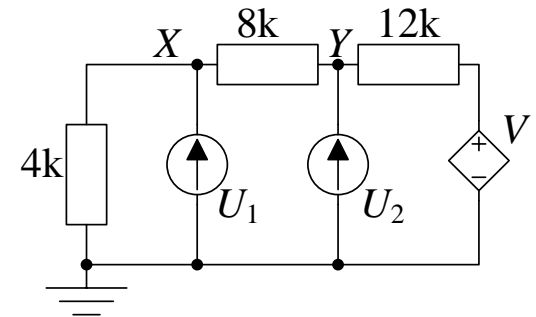
$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V \quad Y = 2U_1 + 6U_2 + \frac{1}{2}V$$



Step 2: Express the dependent source values in terms of node voltages:

$$V = Y - X$$

Step 3: Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X) \Rightarrow \frac{7}{6}X - \frac{1}{6}Y = \frac{10}{3}U_1 + 2U_2 \Rightarrow X = 3U_1 + 3U_2$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X) \Rightarrow \frac{1}{2}X + \frac{1}{2}Y = 2U_1 + 6U_2 \Rightarrow Y = U_1 + 9U_2$$

Note: This is an **alternative** to nodal analysis: you get the same answer.

Single Variable Source

Any current or voltage can be written $X = a_1 U_1 + a_2 U_2 + a_3 U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3} U_1 + \frac{2}{3} U_2$$

Suppose we know $U_2 = 6 \text{ mA}$, then:



$$X = \frac{1}{3} U_1 + 4$$

If all the independent sources except for U_1 have known fixed values, then:

$$X = a_1 U_1 + b$$

where $b = a_2 U_2 + a_3 U_3 + \dots$

This has a straight line graph.

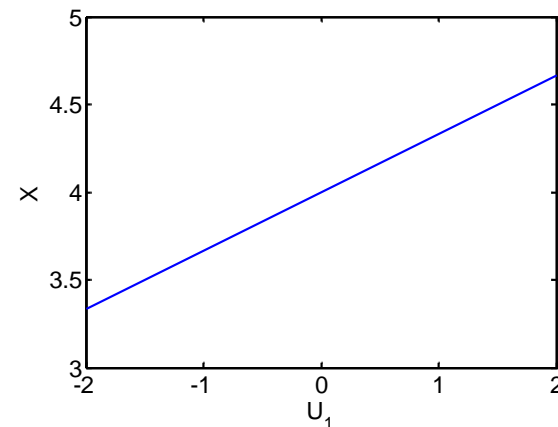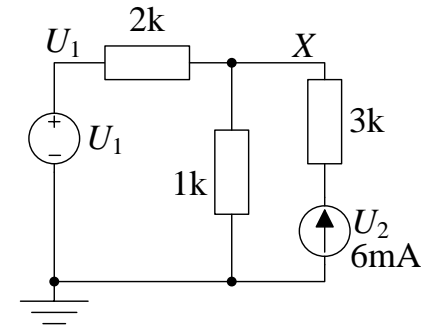

Superposition and Power

The power absorbed (or *dissipated*) by a component always equals VI where the measurement directions of V and I follow the passive sign convention.

For a resistor $VI = \frac{V^2}{R} = I^2 R$


Power in resistor is $P = \frac{(U_1+U_2)^2}{10} = 6.4 \text{ W}$

Power due to U_1 alone is $P_1 = \frac{U_1^2}{10} = 0.9 \text{ W}$

Power due to U_2 alone is $P_2 = \frac{U_2^2}{10} = 2.5 \text{ W}$

$P \neq P_1 + P_2 \Rightarrow$ **Power does not obey superposition.**

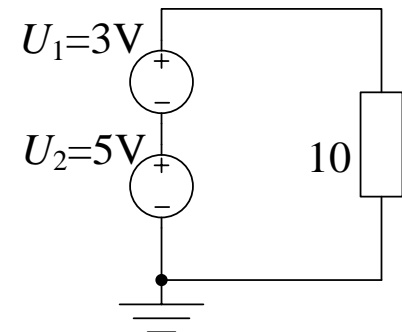You must use superposition to calculate the total V and/or the total I and then calculate the power.



Proportionality

From the linearity theorem, all voltages and currents have the form $\sum a_i U_i$ where the U_i are the values of the independent sources.

If you multiply *all* the independent sources by the same factor, k , then all voltages and currents in the circuit will be multiplied by k .

The power dissipated in any component will be multiplied by k^2 .

Special Case:

If there is only one independent source, U , then all voltages and currents are proportional to U and all power dissipations are proportional to U^2 .

Summary

- **Linearity Theorem:** $X = \sum_i a_i U_i$ over all independent sources U_i
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
 - Zero-value voltage and current sources
 - Dependent sources - treat as independent and add dependency as an extra equation
- If all sources are fixed except for U_1 then all voltages and currents in the circuit have the form $aU_1 + b$.
- Power **does not obey** superposition.
- **Proportionality:** multiplying all sources by k multiplies all voltages and currents by k and all powers by k^2 .

For further details see Hayt Ch 5.